
Breadboard

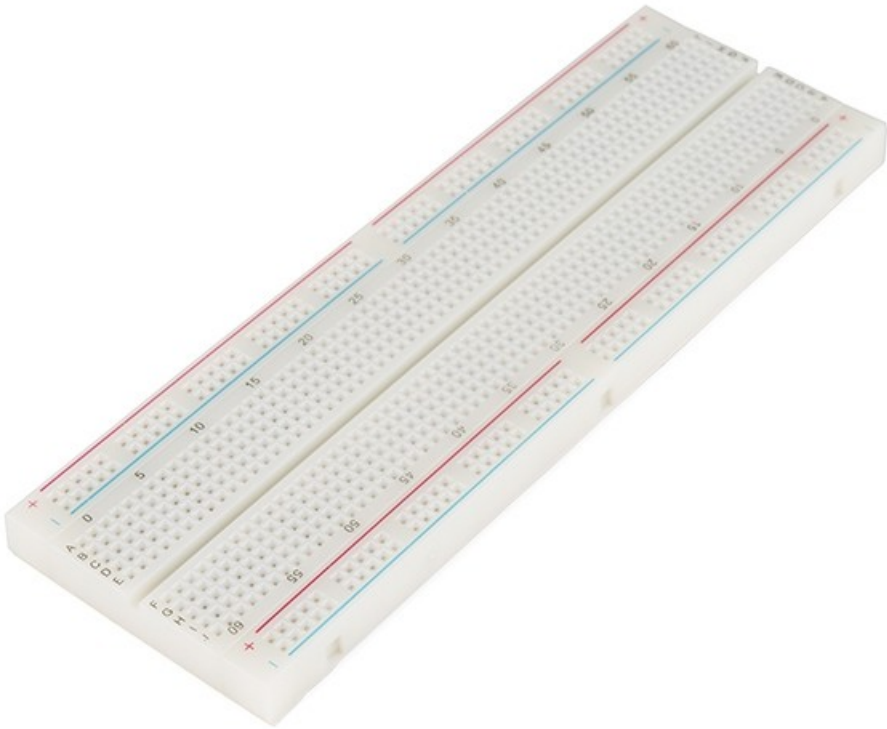- Build circuits without soldering
- Each row of 5 holes is connected
- The centre gap separates the sides




Resistor

- Limits current
- Protects the LED
- Works either way round




330 Ω

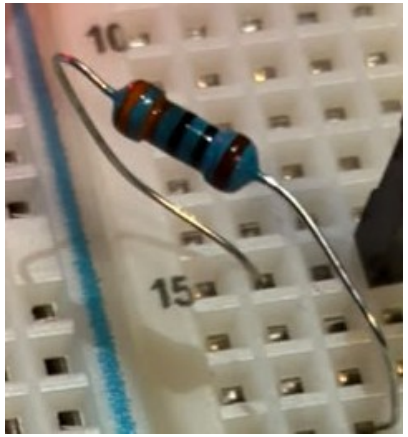

LED & push button

LED

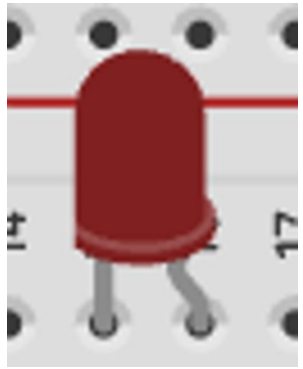- Current flows one way
- Anode (+): long leg
- Cathode (−): short leg / flat side




Push button

- Press to complete the circuit
- Release to break the circuit




Circuit 1: Basic LED

Tinkercad

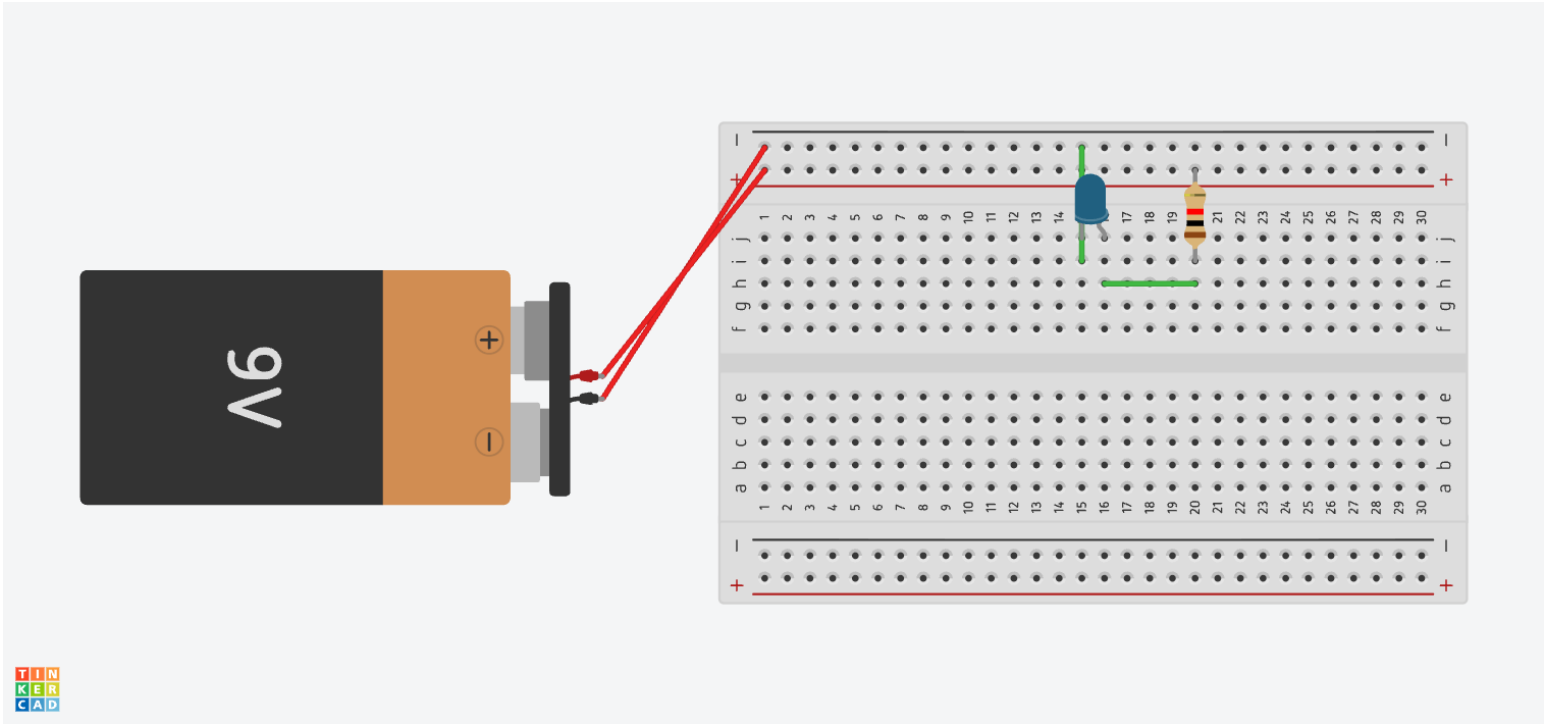


Physical build

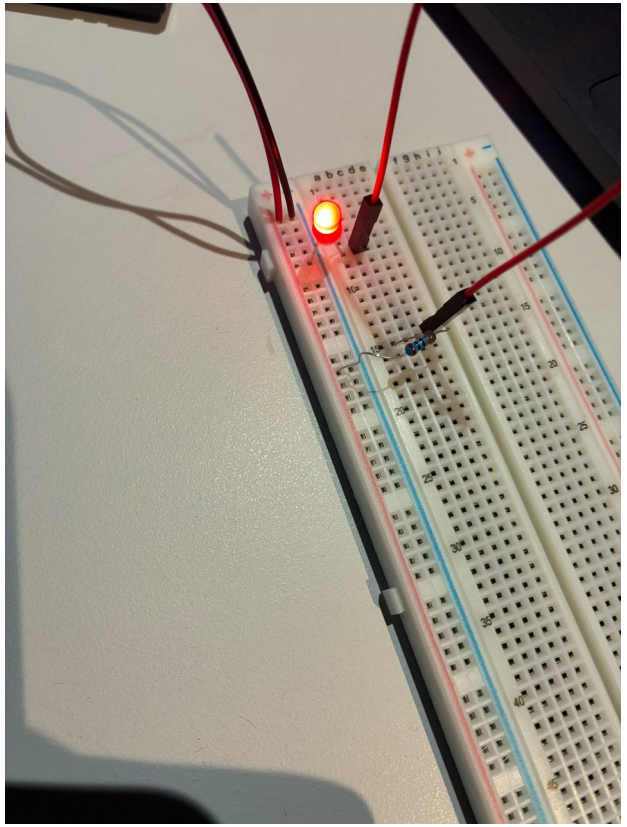

Circuit 2: Push-button LED

Tinkercad

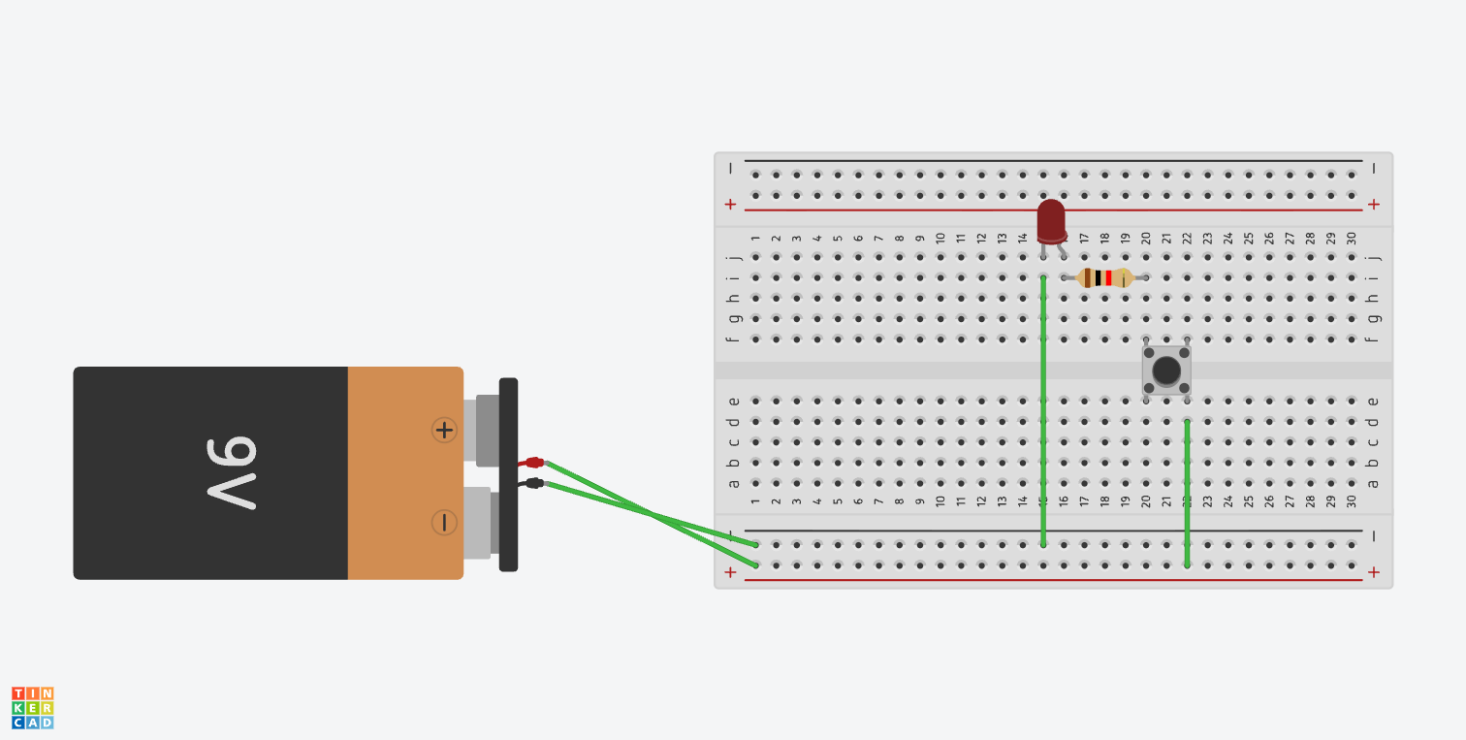

Physical build

